 


CS2022 COMPUTER ARCHITECTURE

Project 2

MICROCODED INSTRUCTIONS SET PROCESSOR



Submitted To: Mr. Michael Manzke

Submitted By: Kavın Gupta
17317505


The VHDL codes are in filenames given corresponding to the components.

COMPONENTS REQUIRED:

1. Register:

Register.vhd


Register_tb.vhd

 

2. Decoder:

Decoder_4to9.vhd


Decoder_tb.vhd

 

3. Multiplexer 2 to1

Mux_2to1.vhd

Mux2_tb.vhd

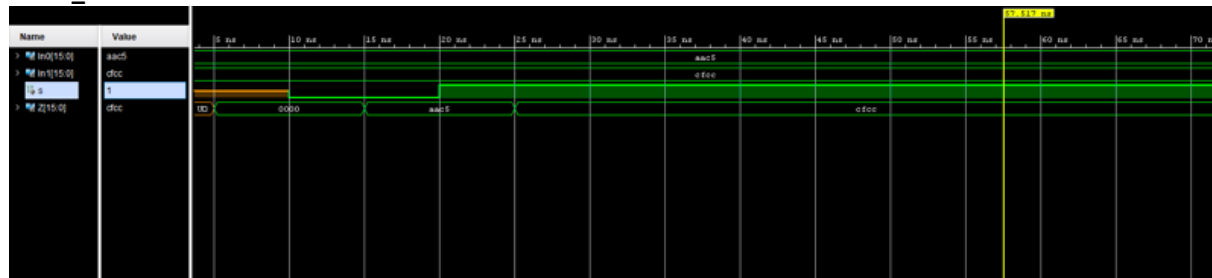

4. Multiplexer 2 to 16

Mux_2to16.vhd

NO testbench required

5. Multiplexer 2 to 8

Mux2to8.vhd

Mux2to8_TB.vhd



6. Multiplexer 3 to 1


Mux_3to1.vhd


No test bench required as it used in Barrel shifter and it is shown working below.

7. Multiplexer 8 to 1


Mux8to1.vhd

Mux8to1_TB.vhd

 

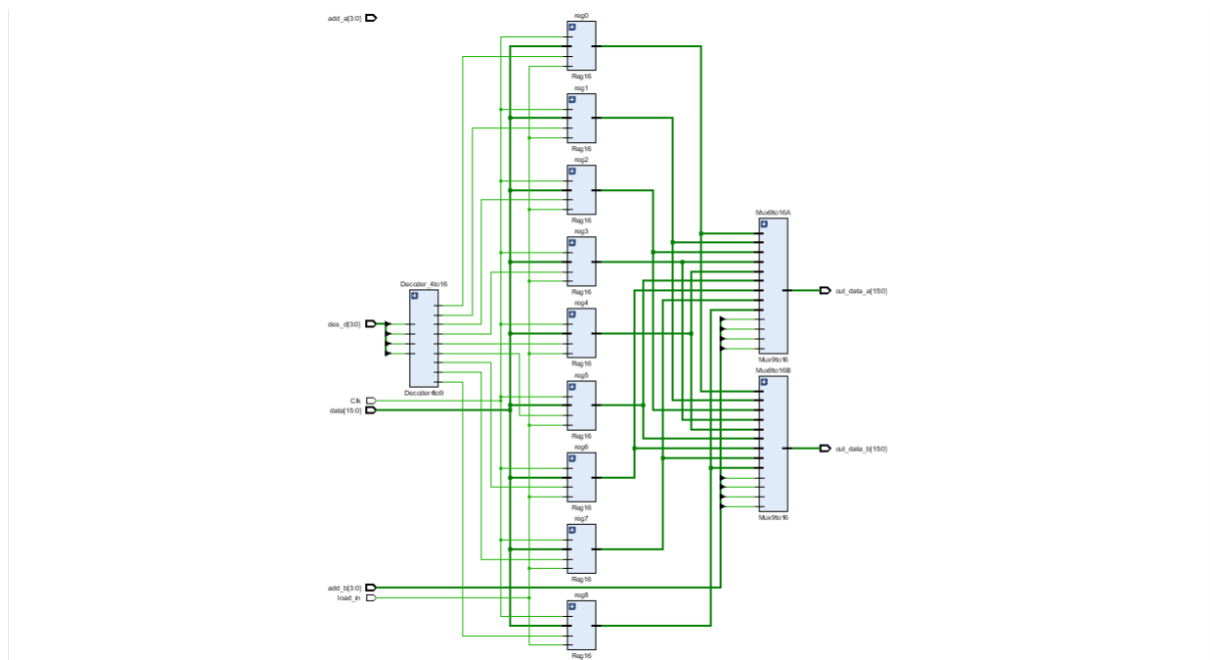


Schematic of Register File

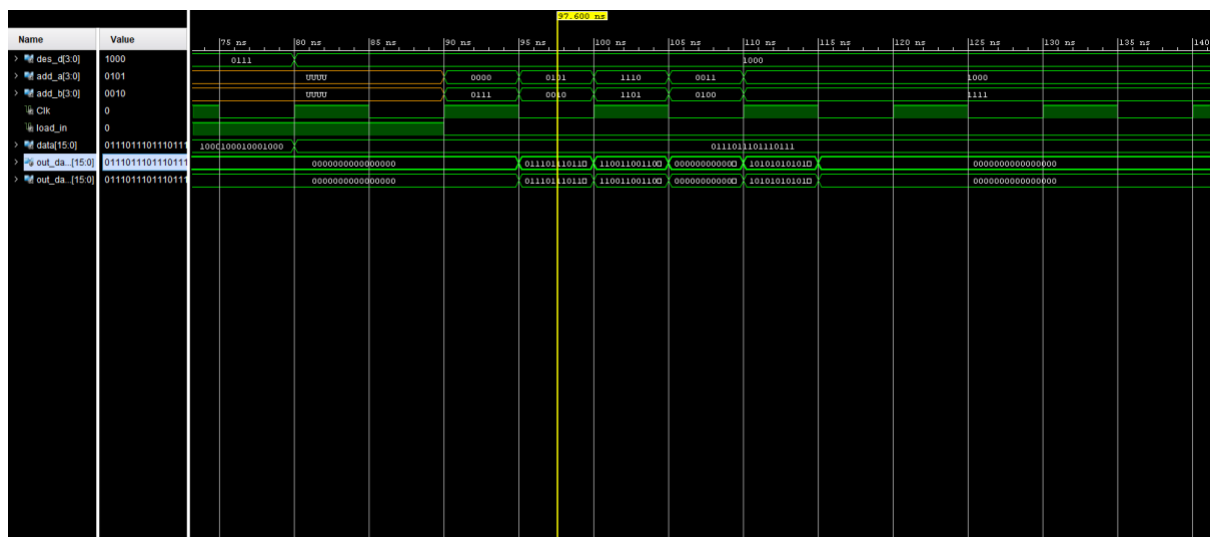

10.Full Adder

Full-adder.vhd

Fulladder_tb.vhd

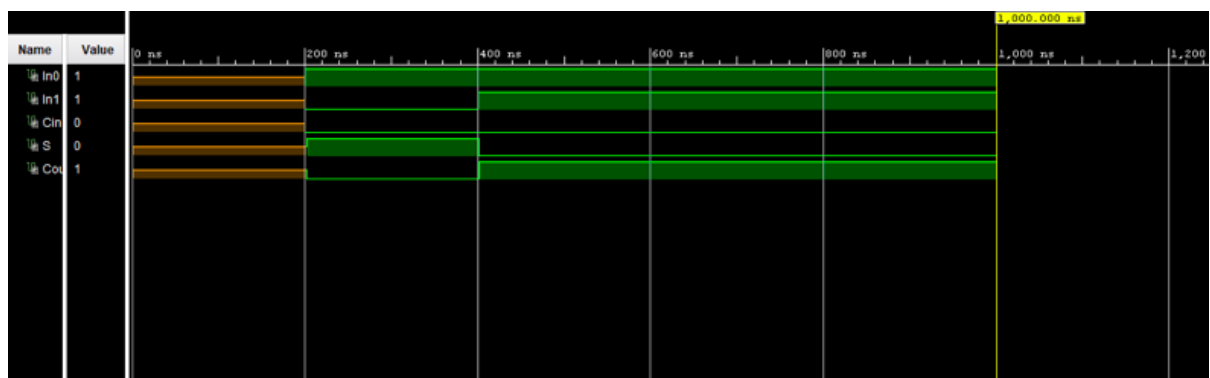


11. Ripple Adder

Ripple_adder.vhd

No test bench required as full adders are shown working and ripple adder is shown working below.

12. Barrel Shifter

Barrel_shifter.vhd

 

Schematic of Barrel Shifter


No test bench Required as it is shown working below.

13.Arithmetic Logic Unit

ALU_16bit.vhd

Logic_circuit_1.vhd

Logic_circuit_2.vhd

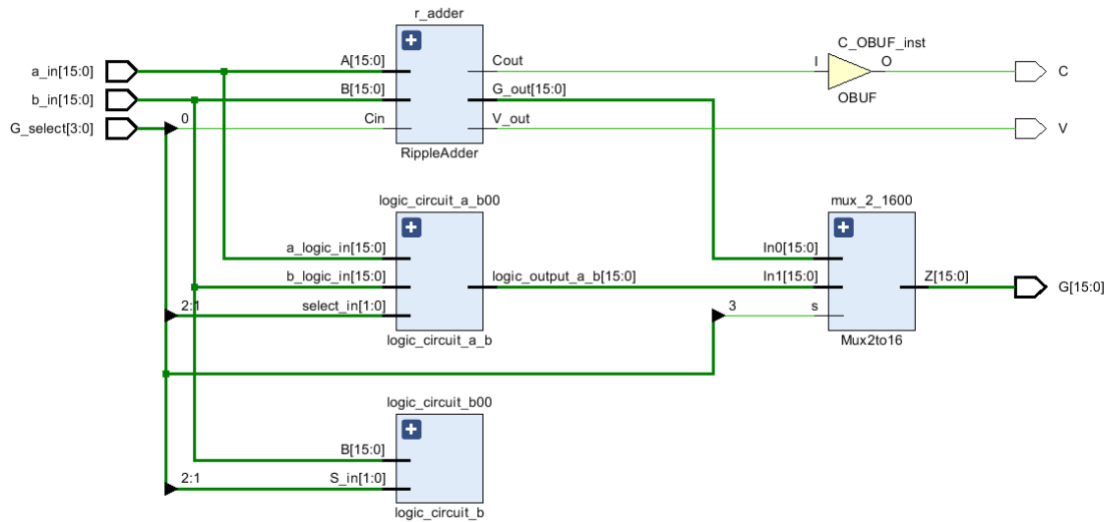


Schematic for Arithmetic Logic Unit

No testbench Required

14.Program Counter

Program_counter.vhd


Program_counter_tb.vhd

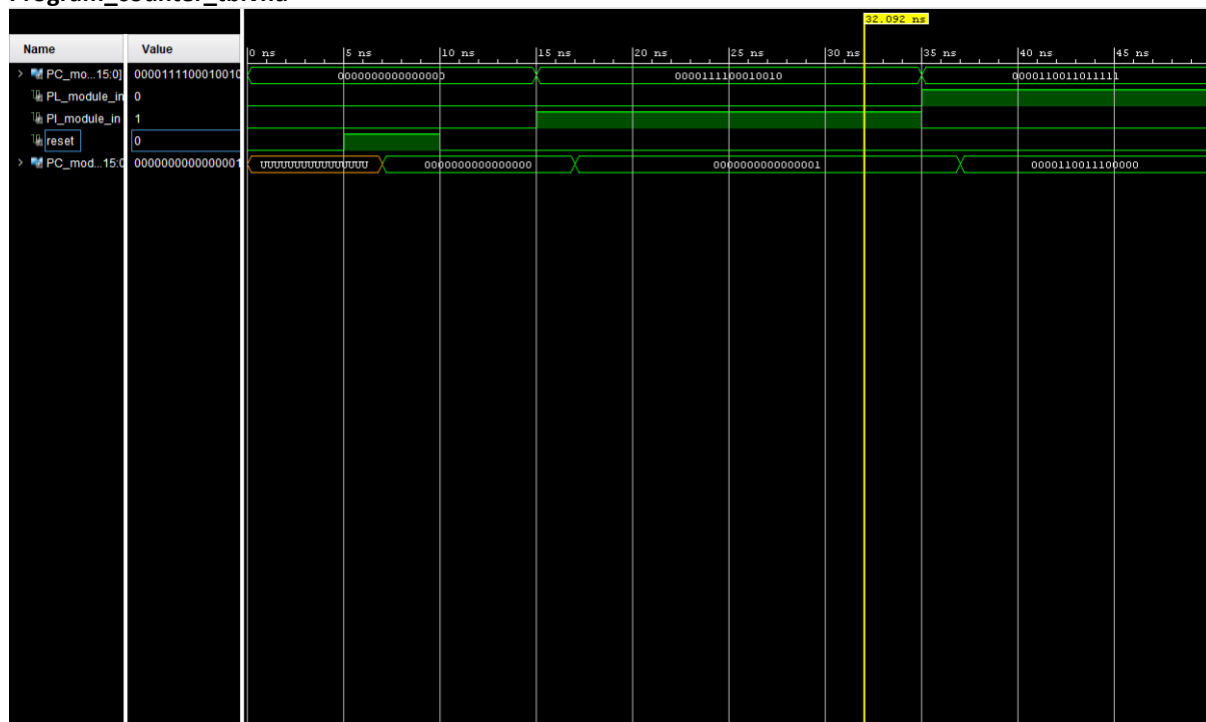

15. Extended program Counter

Extended_program_counter.vhd


Extended_program_counter_tb.vhd

 

16. Zero fill

Zero_fill.vhd

Zero_fill_tb.vhd

 

17. Opcode

Instructions.vhd


Instruction_tb.vhd



18.Control Memory

Control_memory.vhd


Controlmemory_tb.vhd

 

19.Control Address Register

Control_address_reg.vhd

CAR_tb.vhd

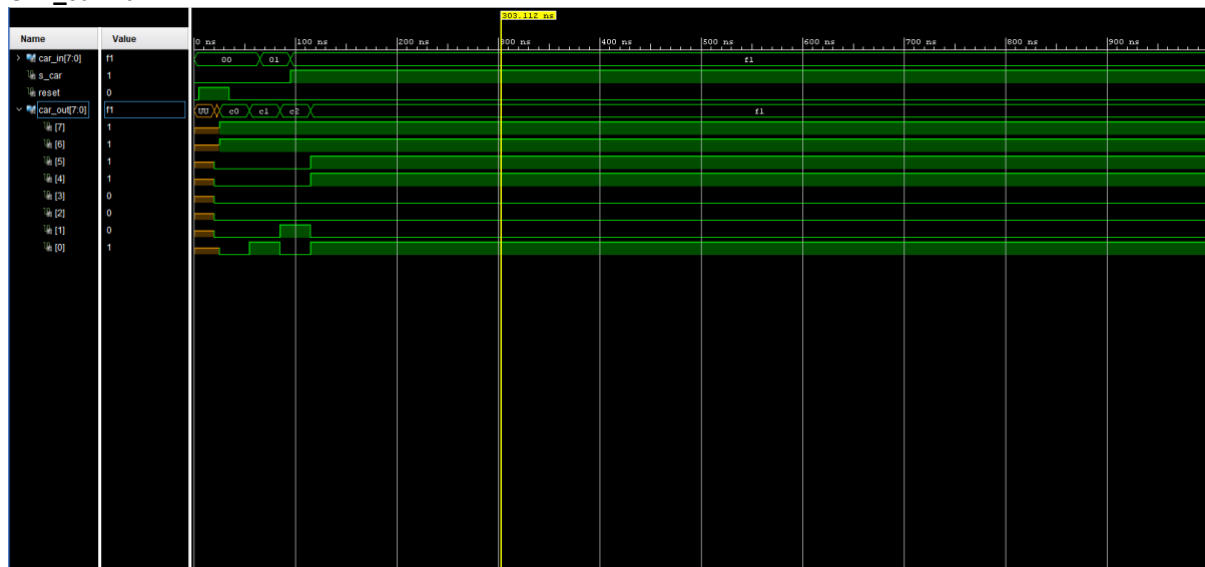

20.Memory


Memory.vhd

Memory_tb.vhd



21.Functional Unit

Functional_unit.vhd

 


Schematic for Functional Unit


22.Data path

Datapath.vhd

Datapath_tb.vhd

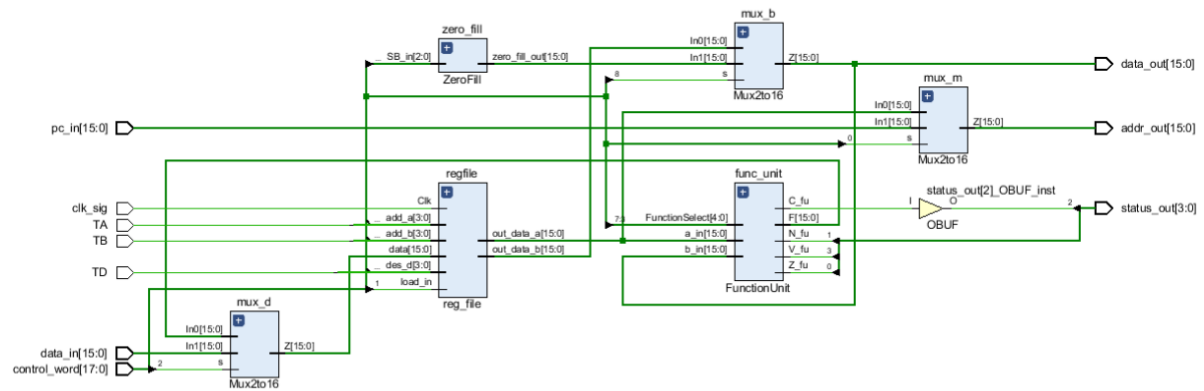


Schematic of Datapath

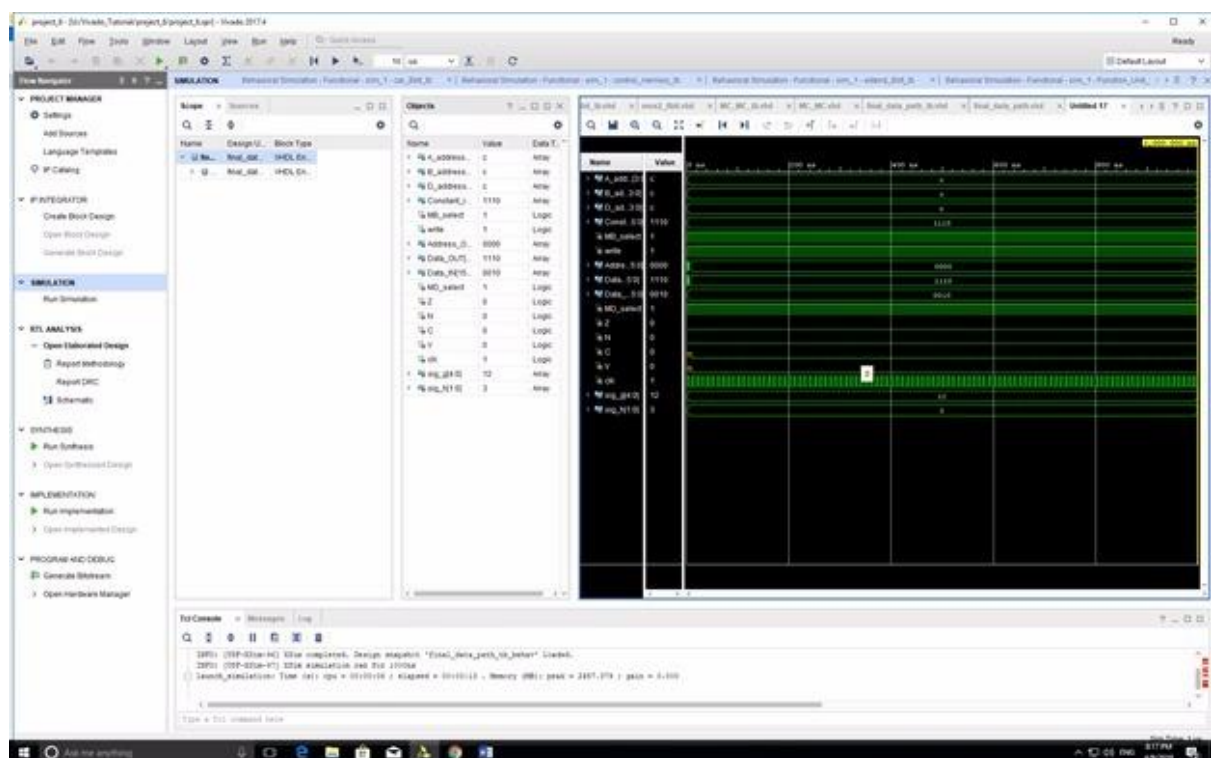

23. Microprogram controller

Microprogrammer_controller.vhd

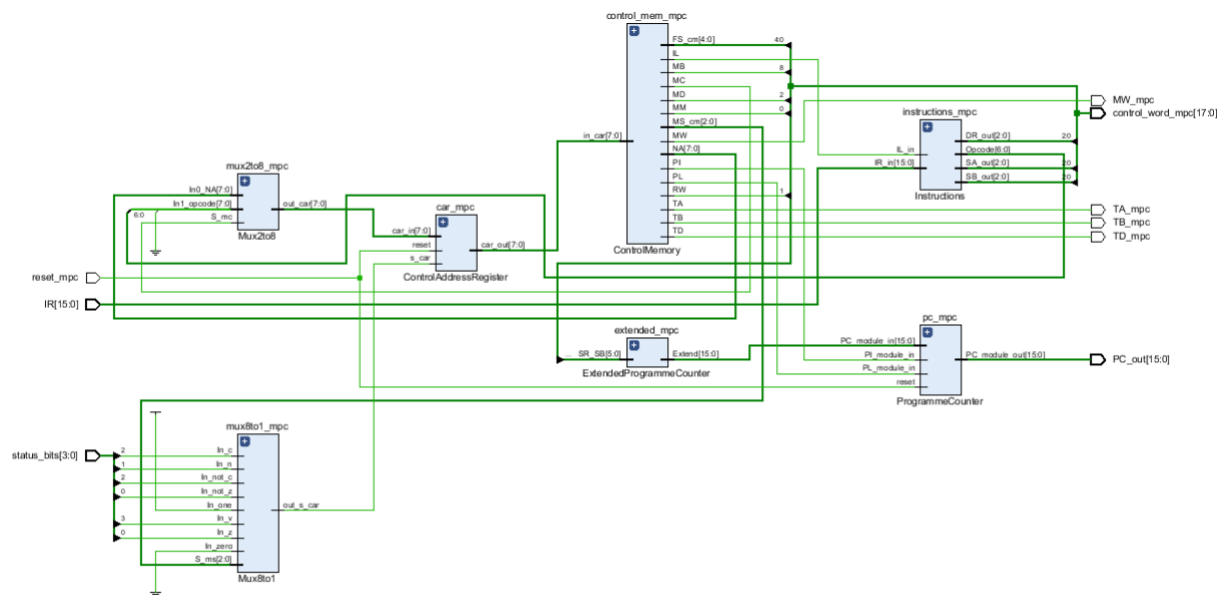


Schematic of Micro Program Control


24. Final


Proj2.vhd

Proj_tb.vhd

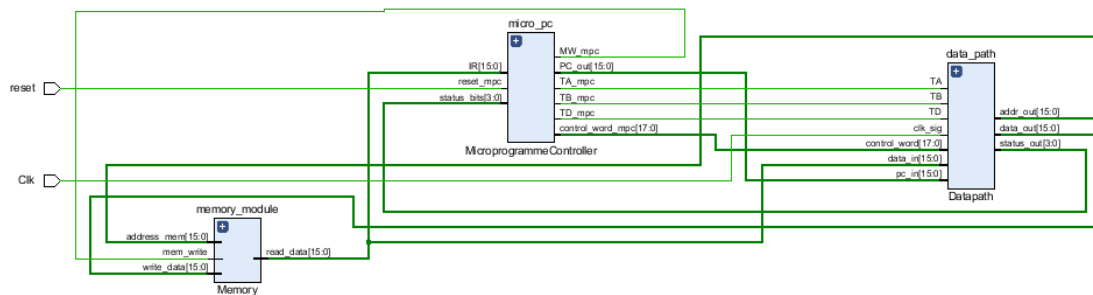

Schematic Overall

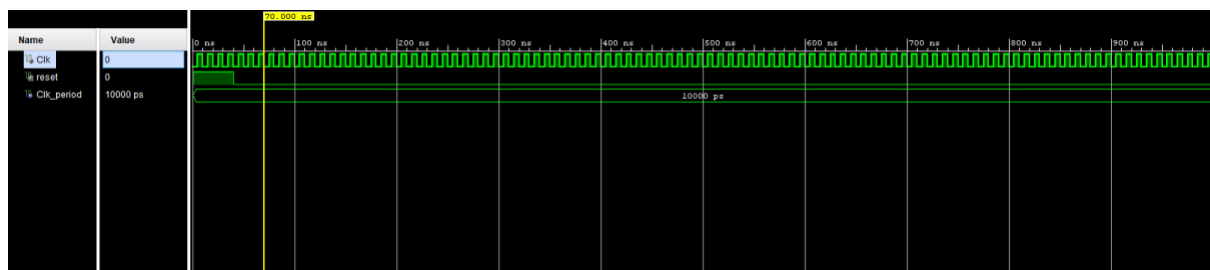

 

This testbench shows the output of registers in the final as the operations are being performed.

The test benches show the result of operands performed by each component with the arithmetic state machine.

With expansion of register file from the previous project, Memory and Control Memory have been added with sized 512X16 and 256X28, each with 16-bit width buses that utilize 9 least significant bits of addresses provided in order to index to the 512-bit memory size.

Microprogram Operations have been implemented for control memory. Each change and resulting operation in time via the register test bench is reflected by loading, add Immediate operand (ADI), load to register (LDR), increment (INC), store (STR), add (ADD), inverse(NOT), unconditional branch (BCH) and conditional branch (BXX). These pertain to modify the content of registers in memory at given time intervals, and more easily seen in the control memory.